 


## Top Level Block Diagram:



---

**Verilog Code:**

```
module DE1_SoC(CLOCK_50, SW, LEDR, KEY, HEX0);
    input CLOCK_50;
    input [9:0] SW;
    input [3:0] KEY;
    output logic [9:0] LEDR;
    output logic [6:0] HEX0;

    assign LEDR[0] = 1'b0;          //skip LEDR[0]
    //connecting wires
    wire right,left;               //used to connect FSMs on left to right

    // buttons for the two different players
    userInput player1 (.Clock(CLOCK_50) , .Reset(SW[9]), .pressed(~KEY[0]), .set(right));
//player 1 presses KEY[0]
    userInput player2 (.Clock(CLOCK_50) , .Reset(SW[9]), .pressed(~KEY[3]), .set(left));
//player 2 presses KEY[3]

    //player1 set value is true when rightmost input is true (player 1 = right)
    //player2 set value is true when leftmost input is true (player 2 = left)

    // instantiations of normal lights and center lights (skips LEDR[0])
    normalLight n1(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LEDR[2]),
.NR(1'b0), .lightOn(LEDR[1]));
    normalLight n2(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LEDR[3]),
.NR(LEDR[1]), .lightOn(LEDR[2]));
    normalLight n3(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LEDR[4]),
.NR(LEDR[2]), .lightOn(LEDR[3]));
    normalLight n4(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LEDR[5]),
.NR(LEDR[3]), .lightOn(LEDR[4]));

    centerLight c1(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LEDR[6]),
.NR(LEDR[4]), .lightOn(LEDR[5]));

    normalLight n6(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LEDR[7]),
.NR(LEDR[5]), .lightOn(LEDR[6]));
    normalLight n7(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LEDR[8]),
.NR(LEDR[6]), .lightOn(LEDR[7]));
```

```

        normalLight n8(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(LED[9]),
.NR(LED[7]), .lightOn(LED[8]));
        normalLight n9(.Clock(CLOCK_50), .Reset(SW[9]), .L(left), .R(right), .NL(1'b0),
.NR(LED[8]), .lightOn(LED[9]));

        //checksWinner to display on hex display
        checkWinner whoWon(.rightMostLight(LED[9]), .leftMostLight(LED[1]), .left(KEY[3]),
.right(KEY[0]), .Reset(SW[9]), .winLight(HEX0)); //leftMostLight: LED[9], rightMostLight:
LED[1]

```

```

endmodule

```

```

// divided_clocks[0] = 25MHz, [1] = 12.5MHz, [23] = 3Hz, [24] 1.5Hz,
// [25] = 0.75 Hz
module clock_divider (clock, divided_clocks);
    input clock;
    output [31:0] divided_clocks;
    reg [31:0] divided_clocks;

```

```

    initial
        divided_clocks <= 0;

    always @(posedge clock)
        divided_clocks <= divided_clocks + 1;

```

```

endmodule

```

```

module centerLight (Clock, Reset, L, R, NL, NR, lightOn);
    input Clock, Reset;
    input  L, R, NL, NR;
    output logic lightOn;

```

```

    // L is true when left key is pressed
    // R is true when the right key is pressed
    // NL is true when the light on the left is on
    // NR is true when the light on the right is on
    //      lightOn is true -- centerLight is on

```

```

logic PS, NS;
parameter off = 1'b0, on = 1'b1;

always @(*)
    case(PS)
        off:    if (NL & R)          NS = on;
                else if (NR & L)     NS = on;
                else                 NS = off;
        on:    if (R ^ L) NS = off;
                else                 NS = on;
        default: NS = 1'bx;
    endcase

always @(*)
    case(PS)
        off: lightOn = off;
        on:  lightOn = on;
        default: lightOn = 1'bx;
    endcase

always @(posedge Clock)
    if (Reset)
        PS <= on; // reset should turn the center light on
    else
        PS <= NS;

endmodule

module centerLight_testbench();

    logic Clk, Reset;
    logic [9:0] LEDR;
    logic [9:0] SW;
    logic NL, NR, L, R;

    //instantiating centerLight module for test
    centerLight dut(.Clock(Clk), .Reset(Reset), .L(L), .R(R), .NL(NL), .NR(NR),
    .lightOn(LED[5]));

    parameter CLOCK_PERIOD = 100;

    initial Clk = 1;
    always begin

```

```

        #(CLOCK_PERIOD/2);
        Clk = ~Clk;
    end
    // Set up the inputs to the design. Each line is a clock cycle.
    initial begin

        Reset <= 1; @(posedge Clk);
                                @(posedge Clk);

        Reset <= 0;  @(posedge Clk);
                                @(posedge Clk);

        L <= 1;      @(posedge Clk);
                                @(posedge Clk);

        NR <= 1;      @(posedge Clk);
                                @(posedge Clk);

        NR <= 0;      @(posedge Clk);
                                @(posedge Clk);

        L <= 0;      @(posedge Clk);
                                @(posedge Clk);

        R <= 1;      @(posedge Clk);
                                @(posedge Clk);

        NL <= 1;     @(posedge Clk);
                                @(posedge Clk);

        NL <= 0;     @(posedge Clk);
                                @(posedge Clk);

        R <= 0;      @(posedge Clk);
                                @(posedge Clk);

        $stop;
    end
endmodule //centerLight_testbench

module normalLight (Clock, Reset, L, R, NL, NR, lightOn);
    input Clock, Reset;
    // L is true when left key is pressed
    // R is true when the right key is pressed
    // NL is true when the light on the left is on

```

```
// NR is true when the light on the right is on
//      lightOn is true -- normalLight is on
```

```
/**FSM Logic Block for normalLight**
//see notes for centerLight, they are mostly the same
```

```
input L, R, NL, NR;
logic PS, NS;
parameter off = 1'b0, on = 1'b1;
// when lightOn is true, the normal light should be on.
output reg lightOn;
```

```
// while
always @(*)
case(PS)
    off:    if (NL & R) NS = on;
            else if (NR & L) NS = on;
            else NS = off;
    on:     if (R ^ L) NS = off;
            else NS = on;
    default: NS = 1'bx;
endcase
```

```
always @(*)
case(PS)
    off: lightOn = 0;
    on:  lightOn = 1;
    default: NS = 1'bx;
endcase
```

```
always @(posedge Clock)
    if (Reset)
        PS <= off; // normal light should be turned off when reset
    else
        PS <= NS;
```

```
endmodule //normalLight
```

```
module normalLight_testbench();
    logic clk, Reset;
    logic LEDR[3];
    logic L, R, NL, NR;
```

```
normalLight dut (.Clock(clk), .Reset(Reset), .L(L), .R(R), .NL(NL), .NR(NR),  
.lightOn(LED[3]));
```

```
//Set up the clock.
```

```
parameter CLOCK_PERIOD = 100;
```

```
initial begin
```

```
    clk <= 0;
```

```
    forever #(CLOCK_PERIOD/2) clk <= ~clk;
```

```
end
```

```
//Set up the inputs to the design. Each line is a clock cycle.
```

```
initial begin
```

```
    Reset <= 1;
```

```
    @(posedge clk);
```

```
    @(posedge clk);
```

```
    Reset <= 0;
```

```
    @(posedge clk);
```

```
    @(posedge clk);
```

```
L<=1;
```

```
    @(posedge clk);
```

```
    @(posedge clk);
```

```
NR <= 1;
```

```
    @(posedge clk);
```

```
    @(posedge clk);
```

```
NR <= 0;
```

```
    @(posedge clk);
```

```
    @(posedge clk);
```

```
    L <= 0;
```

```
    @(posedge clk);
```

```

        @(posedge clk);

                                R <= 1;
    @(posedge clk);

        @(posedge clk);

                                NL <= 1;                                @(posedge
clk);

        @(posedge clk);

                                NL <= 0;
    @(posedge clk);

        @(posedge clk);

                                R <= 0;
    @(posedge clk);

        @(posedge clk);
    $stop; //End the simulation.
end
endmodule //normalLight_testbench

//metastability (user input)
module userInput(Clock, Reset, pressed, set);
    input Clock, Reset;
    input pressed;
    output reg set;
    logic [1:0] PS, NS;
    parameter [1:0] on = 2'b00, hold = 2'b01, off = 2'b10;

    always @(*)
    case(PS)
        on:    if (pressed) NS = hold;
              else NS = off;
        hold:  if (pressed) NS = hold;
    endcase

```



```

        else NS = off;
    off:    if (pressed) NS = on;
            else NS = off;
    default: NS = 2'bxx;
endcase

always @(*)
case(PS)
    on: set = 1;
    hold: set = 0;
    off: set = 0;
    default: set = 1'bx;
endcase

always_ff @(posedge Clock)
    if (Reset)
        PS <= off;
    else
        PS <= NS;

endmodule

module checkWinner(leftMostLight, rightMostLight, left, right, Reset, winLight);
    input leftMostLight, rightMostLight, left, right, Reset;
    parameter b1 = 7'b1111001, b2 = 7'b0100100, b0 = 7'b1000000;
    logic winL, winR;
    output logic [6:0] winLight;

    assign winL = leftMostLight & left & ~right; //set up win condition for player 1
    assign winR = rightMostLight & right & ~left; //and player 2
    always @(*)
    begin
        if (winL) // if player 2 wins
            winLight = b2;
        else if (winR) // if play 1 wins
            winLight = b1;
        else if (Reset | ~winL & ~winR) //game reset
            winLight = b0;
    end

endmodule

endmodule

module DE1_SoC_testbench(); //CLOCK_50, KEY, SW, LEDR, HEX0
    logic CLOCK_50;

```

```
logic [9:0] SW;  
logic [3:0] KEY;  
logic [9:0] LEDR;  
logic [6:0] HEX0;
```

```
//instantiating main module  
DE1_SoC dut (CLOCK_50, SW, LEDR, KEY, HEX0);
```

```
initial CLOCK_50 = 1;  
parameter CLOCK_PERIOD = 100;
```

```
always begin  
    #(CLOCK_PERIOD/2);  
    CLOCK_50 = ~CLOCK_50;  
end
```

```
initial begin  
    //only toggles with the player 1&2 keys  
    SW[9] <= 1; @(posedge CLOCK_50);  
    @(posedge CLOCK_50);  
    SW[9] <= 0;  @(posedge CLOCK_50);  
    @(posedge CLOCK_50);  
  
    SW[8:0] <= 9'b111000000; @(posedge CLOCK_50);
```

```
KEY[0] <= 1;      @(posedge CLOCK_50); //checking player 1 win  
KEY[0] <= 0;      @(posedge CLOCK_50);  
KEY[0] <= 1;      @(posedge CLOCK_50);  
KEY[0] <= 0;      @(posedge CLOCK_50);  
KEY[0] <= 1;      @(posedge CLOCK_50);  
KEY[0] <= 0;      @(posedge CLOCK_50);  
KEY[0] <= 1;      @(posedge CLOCK_50);  
KEY[0] <= 0;      @(posedge CLOCK_50);  
KEY[0] <= 1;      @(posedge CLOCK_50);  
KEY[0] <= 0;      @(posedge CLOCK_50);  
KEY[0] <= 1;      @(posedge CLOCK_50);    //1
```

```
SW[9] <= 1;      @(posedge CLOCK_50); //reset  
    @(posedge CLOCK_50);  
SW[9] <= 0;      @(posedge CLOCK_50);  
    @(posedge CLOCK_50);
```

```

KEY[3] <= 1;      @(posedge CLOCK_50); //checking player 2 win
KEY[3] <= 0;      @(posedge CLOCK_50);
KEY[3] <= 1;      @(posedge CLOCK_50);
KEY[3] <= 0;      @(posedge CLOCK_50);
KEY[3] <= 1;      @(posedge CLOCK_50);
KEY[3] <= 0;      @(posedge CLOCK_50);
KEY[3] <= 1;      @(posedge CLOCK_50);
KEY[3] <= 0;      @(posedge CLOCK_50);
KEY[3] <= 1;      @(posedge CLOCK_50);
KEY[3] <= 0;      @(posedge CLOCK_50);
KEY[3] <= 1;      @(posedge CLOCK_50);

```

```

SW[9] <= 1;      @(posedge CLOCK_50); //reset
                  @(posedge CLOCK_50);
SW[9] <= 0;      @(posedge CLOCK_50);
                  @(posedge CLOCK_50);

```

```

$stop;

```

```

end
endmodule

```

## Resource Utilization by Entity:

### Analysis & Synthesis Resource Utilization by Entity

<<Filter>>										
	Compilation Hierarchy Node	Combinational ALUTs	Dedicated Logic Registers	Block Memory Bits	DSP Blocks	Pins	Virtual Pins	Full Hierarchy Name	Entity Name	Library Name
1	▼  DE1_SoC	18 (0)	13 (0)	0	0	32	0	DE1_SoC	DE1_SoC	work
1	centerLightc1	1 (1)	1 (1)	0	0	0	0	DE1_SoC centerLightc1	centerLight	work
2	checkWinner:whoWon	3 (3)	0 (0)	0	0	0	0	DE1_SoC checkWinner:whoWon	checkWinner	work
3	normalLightn1	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn1	normalLight	work
4	normalLightn2	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn2	normalLight	work
5	normalLightn3	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn3	normalLight	work
6	normalLightn4	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn4	normalLight	work
7	normalLightn6	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn6	normalLight	work
8	normalLightn7	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn7	normalLight	work
9	normalLightn8	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn8	normalLight	work
10	normalLightn9	1 (1)	1 (1)	0	0	0	0	DE1_SoC normalLightn9	normalLight	work
11	userInput:player1	3 (3)	2 (2)	0	0	0	0	DE1_SoC userInput:player1	userInput	work
12	userInput:player2	3 (3)	2 (2)	0	0	0	0	DE1_SoC userInput:player2	userInput	work